

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY**PDDC SEM-IV Examination-Nov-2011****Subject code: X41103****Date: 25/11/2011****Subject Name: Integrated Circuit and application****Time: 2.30 pm -5.00 pm****Total marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain the Characteristics of Ideal Op-amp (03) **07**
 Short Note : Comparator circuit using Op-amp (04)
- (b) Derive the expression for voltage gain, input resistance, output resistance and bandwidth of non inverting amplifier using Op-amp with negative voltage series feedback **07**
- Q.2** (a) Explain application of Op-amp (Inverting Configuration) as Summing, Scaling and averaging circuit **07**
- (b) Define following terms 1.CMRR 2.PSRR 3.Slew Rate **07**
 4.Input Offset voltage 5.Input Offset current 6.Input bias current 7.Equivalent input noise voltage and current
- OR**
- (b) Draw Circuit diagram of differential amplifier with three op-amp and derive expression for its output signal as function of input signal **07**
- Q.3** (a) Draw Circuit diagram of Schmitt trigger by Op-amp and explain it. **07**
- (b) Draw Circuit diagram of Clipper and Clamper by Op-amp and explain it. **07**
- OR**
- Q.3** (a) Draw and explain working Op-amp based half wave rectifier circuit. How is it better in performance compared to half wave rectifier circuit without Op-amp **07**
- (b) Draw and Explain Working Op-amp based log amplifier **07**
- Q.4** (a) Explain working of 555 based astable multivibrator. **07**
- (b) What are Different types of Voltage regulator? Discuss LM317 based adjustable voltage regulator **07**
- OR**
- Q.4** (a) Explain working of 555 based monostable multivibrator. Design same for output pulse width of 10ms. **07**
- (b) Draw and explain Triangular and Saw tooth wave generator circuit using Op-amp **07**
- Q.5** (a) Design a Differentiator circuit by using Op-amp to differentiate an input signal that varies in frequency from 10 Hz to about 1 KHz. Draw its frequency response **07**
- (b) Draw Circuit diagram of Op-amp based first order Low pass Butterworth filter and explain it **07**
- OR**
- Q.5** (a) Draw Op-amp based Integrator circuit and derive expression for its output voltage in terms of its input voltage **07**
- (b) Draw circuit diagram of Op-amp based first order high pass Butterworth filter and explain it. **07**