

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-1/2 EXAMINATION – WINTER 2017

Subject Code: 110005

Date: 09/01/2018

Subject Name: Elements of Electrical Engineering

Time: 10:30 AM TO 01:00 PM

Total Marks: 70

Instructions:

1. Attempt any questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) State and explain Kirchoff's voltage law and current law with suitable examples **07**
(b) A coil has a resistance of 18Ω when the mean temperature is 20°C and 20Ω when the temperature is 50°C . Find its mean temperature rise when the resistance is 21Ω and the ambient temperature is 15°C . **07**
- Q.2** (a) Derive the expression for charging current in a R-C circuit. Hence, define the time constant of RC circuit. **07**
(b) Obtain the relation $L = (L_1 L_2 - M^2) / (L_1 + L_2 + 2M)$ for the equivalent inductance when two coils are connected in parallel such that the mutually induced emf opposes the self induced emf. **07**
- Q.3** (a) Define capacitance and derive the equation of the same for a parallel plate capacitor with uniform dielectric medium. Also, derive the equation for the energy stored in it. **07**
(b) Explain Faraday's law of electromagnetic induction. Hence explain statically induced e.m.f and dynamically induced e.m.f. **07**
- Q.4** (a) Explain the similarities & dissimilarities between electric and magnetic circuits. **07**
(b) Define i. RMS value ii. Average value for an a.c waveform. Write the mathematical expression for the same. Hence, define also Form Factor and Peak Factor. **05**
02
- Q.5** (a) Derive the expression for current through a series connected R- L circuit when supplied by a.c sinusoidal voltage. Draw the vector diagram. Also derive the expression of average power consumption in this circuit over 1 cycle **07**
(b) A circuit contains a resistance of 4Ω , inductance of 0.5 H and a variable capacitance C connected in series across 100 V , 50 Hz supply. Calculate i). The value of capacitance to produce resonance ii). Voltage and current across C at resonance iii). Q factor of the circuit. **07**
- Q.6** (a) Derive the relation between line voltage and phase voltage, line current and phase current in a star connected electric circuit. **07**
(b) Draw the diagram and explain the working of i. Staircase wiring ii. Parallel or domestic wiring. **07**
- Q.7** (a) Explain the two wattmeter method to measure power in a balanced 3 phase circuit. **07**
(b) Explain the working of ELCB and MCB. **07**
